MCQ Type for Basic electrical Engg.

Prepared By :- Sushil Swain (Asst. Professor in EE dept.)

1. Electrostatics is a branch of electricity concerned with

- (a) Energy flowing across a gap between conductors
- (b) Charges at rest
- (c) Charges in motion

(d) Energy in the form of charges

Ans: B

2. Four 2 µF capacitors are connected in series. The equivalent capacitance is

- (a) 8 µF
- (b) 0.5 µF
- (c) 2 µF
- (d) 6 µF

Ans: B

3. State which of the following is false.

The capacitance of a capacitor

- (a) Is proportional to the cross-sectional area of the plates
- (b) Is proportional to the distance between the plates
- (c) Depends on the number of plates
- (d) Is proportional to the relative permittivity of the dielectric

Ans: B

4. The capacitance of a capacitor is the ratio

- (a) Charge to potential difference between plates
- (b) Potential difference between plates to plate spacing
- (c) Potential difference between plates to thickness of dielectric
- (d) Potential difference between plates to charge

Ans: A

5. Which of the following statement is false?

(a) An air capacitor is normally a variable type

- (b) A paper capacitor generally has a shorter service life than most other types of
- capacitor
- (c) An electrolytic capacitor must be used only on a.c. supplies

(d) Plastic capacitors generally operate satisfactorily under conditions of high temperature **Ans:A**

6.The potential difference across a 10 µF capacitor to charge it with 10mC is

- (a) 10V
- (b) 1 kV
- (c) 1V
- (d) 10V
- Ans: B

7. The energy stored in a $10\mu F$ capacitor when charged to 500V is

- (a) 1.25 mJ
- (b) 0.025 µJ
- (c) 1.25 J
- (d) 1.25 C

Ans: C

8. The capacitance of a variable air capacitor is at maximum when

(a) The movable plates half overlap the fixed plates

(b) The movable plates are most widely separated from the fixed plates

- (c) Both sets of plates are exactly meshed
- (d) The movable plates are closer to one side of the fixed plate than to the other Ans: C

- 9. The unit of magnetic flux density is the:
- (a) Weber
- (b) Weber per metre
- (c) Ampere per metre
- (d) Tesla

Ans: D

10. The charge on a 10 pF capacitor when the voltage applied to it is 10 kV is

- (a) 100 µC
- (b) 0.1 C
- (c) 0.1 µC
- (d) 0.01 µC

Ans: C

11. Four 2 µF capacitors are connected in parallel. The equivalent capacitance is

- (a) 8 µF
- (b) 0.5 µF
- (c) 2 µF
- (d) 6 µF

Ans: A

12. In a series a.c. circuit the voltage across a pure inductance is 12V and the voltage across a pure resistance is 5V. The supply voltage is

- (a) 13V
- (b) 17V
- (c) 7V
- (d) 2.4V

Ans: A

13. Inductive reactance results in a current that

(a) Leads the voltage by 90deg

- (b) Is in phase with the voltage
- (c) Leads the voltage by π rad
- (d) Lags the voltage by $\pi/2$ rad

Ans: D

14. A 10 Ω resistor is connected in parallel with a 15 Ω resistor and the combination in series with a 12 Ω resistor. The equivalent resistance of the circuit is:

- (a) 37Ω
- (b) 18 Ω
- (c) 27 Ω
- (d) 4 Ω

Ans: B

15. The equivalent resistance when a resistor of $(1/3)\Omega$ is connected in parallel with a $(1/4)\Omega$ resistance is:

- (a) 1/7 Ω
- (b) 7Ω
- (c) 1/12 Ω
- (d) 3/4 Ω

Ans: A

16. A 240V, 60W lamp has a working resistance of:

- (a) 1400Ω
- (b) 60Ω

(c) 960Ω

(d) 325Ω

Ans: C

17. The symbol for the unit of temperature coefficient of resistance is:

(a) Ω /°C

(b)Ω

(c) °C

(d) $\Omega / \Omega^{\circ}C$

Ans: D

18. The length of a certain conductor of resistance 100Ω is doubled and its cross-sectional area is halved. Its new resistance is:

- (a) 100Ω
- (b) 200Ω
- (c) 50Ω
- (d) 400Ω

Ans: D

19.Voltage drop is the:

- (a) Maximum potential
- (b) Difference in potential between two points
- (c) Voltage produced by a source
- (d) Voltage at the end of a circuit

Ans: B

20.The largest number of 100W electric light bulbs which can be operated from a 240V supply fitted with a 13A fuse is:

- (a) 2
- (b) 7
- (c) 31
- (d) 18

Ans: C

21. When an atom loses an electron, the atom:

- (a) Becomes positively charged
- (b) Disintegrates
- (c) Experiences no effect at all
- (d) Becomes negatively charged

Ans: A

22. The energy used by a 1.5kW heater in 5 minutes is:

- (a) 5 J
- (b) 450 J
- (c) 7500 J
- (d) 450 000 J

Ans: D

23. The unit of resistivity is:

- (a) ohms
- (b) ohm millimetre
- (c) ohm metre
- (d) ohm/metre

Àns: C

24.A resistor marked as4K7G indicates a value of:

(a) 47Ω ±20%

(b) 4.7Ω k ±20% (c) 0.47Ω ±10%

(d) 4.7 kΩ ±2

Ans: D

25. The resistance of a 2 km length of cable of cross-sectional area $2mm^2$ and resistivity of $2 \times 10^{-8} \Omega$ m is:

- (a) 0.02Ω
- (b) 20Ω
- (c) 0.02mΩ
- (d) 200Ω

Ans: B

26. A piece of graphite has a cross-sectional area of $10mm^2$. If its resistance is 0.1Ω and its resistivity $10 \times 10^8 \Omega m$, its length is:

(a) 10 km

(b) 10 cm

(c) 10 mm

(d) 10 m

Ans: D

27. A nickel coil has a resistance of 13Ω at 50° C. If the temperature coefficient of resistance at 0° C is 0.006/ °C, the resistance at 0°C is:

- (a) 16.9Ω
- (b) 10Ω
- (c) 43.3Ω
- (d) 0.1Ω

Ans: B

28. A coil of wire has a resistance of 10 at 0°C. If the temperature coefficient of resistance for the wire is 0.004/ °C, its resistance at 100°C is:

- (a) 0.4Ω
- (b) 1.4Ω
- (c) 14Ω
- (d) 10Ω

Ans: C

29A colour coding of red-violet-black on a resistor indicates a value of:

- (a) 27Ω ±20%
- (b) 270Ω
- (c) 270Ω ±20%
- (d) 27Ω ±10%

Ans: C

30. An inductance of 10mH connected across a 100V, 50 Hz supply has an inductive reactance of

- (a) 10π
- (b) 1000π
- (c) π
- (d) π H

Ans:C

- 31. The coulomb is a unit of:
- (a) Energy
- (b) Voltage
- (c) Power
- (d) Quantity of electricity

Ans: D

32. A charge of 240 C is transferred in 2 minutes. The current flowing is:

(a) 480A

(b) 120A

(c) 2A

(d) 8A

Ans: C

33. A resistance of 50 k Ω has a conductance of:

- (a) 20S
- (b) 0.02S
- (c) 0.02 mS
- (d) 20 kS

Ans: C

34. Which of the following statements is incorrect?

- (a) $1N = 1 \text{ kgm/s}^2$
- (b) 1V = 1 J/C
- (c) 30mA = 0.03A
- (d) 1 J = 1N/m

Ans:D

35. The power dissipated by a resistor of 10 ohm when a current of 2A passes through it is:

- (a) 0.4W
- (b) 20W
- (c) 40W
- (d) 200W

Ans: C

36. A mass of 1200g is accelerated at 200 cm/s² by a force. The value of the force required is:

- (a) 2.4N
- (b) 2400N
- (c) 240 kN
- (d) 0.24N

Ans: A

37.A current of 2A flows for 10 hour through a 100 ohm resistor. The energy consumed by the resistor is:

- (a) 0.5 kWh
- (b) 4 kWh
- (c) 2 kWh
- (d) 0.02 kWh

Ans:B

38. The unit of quantity of electricity is the:

- (a) volt
- (b) coulomb
- (c) ohm
- (d) joule

Ans: B

39. Electromotive force is provided by:

- (a) Resistance's
- (b) A conducting path
- (c) An electric current
- (d) An electrical supply source

Ans: C

40. The unit of current is the:

- (a) Volt
- (b) Coulomb
- (c) Joule
- (d) Ampere

Ans: D

41. In order that work may be done:

- (a) Two wires are necessary
- (b) The circuit must have a switch
- (c) Coal must be burnt
- (d) A supply of energy is required

Ans: D

42. The ohm is the unit of:

- (a) Charge
- (b) Resistance
- (c) Power
- (d) Current

Ans: B

43. The unit of resistivity is:

- (a) ohms
- (b) ohm millimetre
- (c) ohm metre
- (d) ohm/metre

Ans: C

44.Voltage drop is the:

- (a) Maximum potential
- (b) Difference in potential between two points
- (c) Voltage at the end of a circuit
- (d) Voltage produced by a source

Ans: B

45.A 240V, 60W lamp has a working resistance of:

- (a) 1400 ohm
- (b) 60 ohm
- (c) 960 ohm
- (d) 325 ohm

Ans: C

46.The potential difference across a 10 μF capacitor to charge it with 10mC is

- (a) 10V
- (b) 1 kV
- (c) 1V
- (d) 10V

Ans: B

47. The energy stored in a $10\mu F$ capacitor when charged to 500V is

- (a) 1.25 mJ
- (b) 0.025 µJ
- (c) 1.25 J
- (d) 1.25 C

Ans: C

48. The capacitance of a variable air capacitor is at maximum when

- (a) The movable plates half overlap the fixed plates
- (b) The movable plates are most widely separated from the fixed plates

- (c) Both sets of plates are exactly meshed
- (d) The movable plates are closer to one side of the fixed plate than to the other **Ans: C**
- Ans: C
- 49. The unit of magnetic flux density is the:
- (a) Weber
- (b) Weber per metre
- (c) Ampere per metre
- (d) Tesla

Ans: D

50. The charge on a 10 pF capacitor when the voltage applied to it is 10 kV is

- (a) 100 µC
- (b) 0.1 C
- (c) 0.1 µC
- (d) 0.01 µC

Ans: C

51. Four 2 µF capacitors are connected in parallel. The equivalent capacitance is

- (a) 8 µF
- (b) 0.5 µF
- (c) 2 µF
- (d) 6 µF

Ans: A

52. In a series a.c. circuit the voltage across a pure inductance is 12V and the voltage across a pure resistance is 5V. The supply voltage is

- (a) 13V
- (b) 17V
- (c) 7V
- (d) 2.4V

Ans: A

53. Inductive reactance results in a current that

(a) Leads the voltage by 90deg

- (b) Is in phase with the voltage
- (c) Leads the voltage by $\boldsymbol{\pi}$ rad
- (d) Lags the voltage by $\pi/2\ \text{rad}$

Ans: D

54. A 10 Ω resistor is connected in parallel with a 15 Ω resistor and the combination in series with a 12 Ω resistor. The equivalent resistance of the circuit is:

- (a) 37Ω
- (b) 18 Ω
- (c) 27 Ω
- (d) 4 Ω

Ans: B

55. The equivalent resistance when a resistor of $(1/3)\Omega$ is connected in parallel with a $(1/4)\Omega$ resistance is:

- (a) 1/7 Ω
- (b) 7Ω
- (c) 1/12 Ω
- (d) 3/4 Ω

Ans: A

56. A 240V, 60W lamp has a working resistance of:

- (a) 1400Ω
- (b) 60Ω

(c) 960Ω

(d) 325Ω

Ans: C

57. The symbol for the unit of temperature coefficient of resistance is:

(a) Ω /°C

(b)Ω

 $(c) ^{\circ} C$

(d) Ω /Ω°C

Ans: D

58. The length of a certain conductor of resistance 100Ω is doubled and its cross-sectional area is halved. Its new resistance is:

- (a) 100Ω
- (b) 200Ω
- (c) 50Ω
- (d) 400Ω

Ans: D

59.Voltage drop is the:

- (a) Maximum potential
- (b) Difference in potential between two points
- (c) Voltage produced by a source
- (d) Voltage at the end of a circuit

Ans: B

60.The largest number of 100W electric light bulbs which can be operated from a 240V supply fitted with a 13A fuse is:

- (a) 2
- (b) 7
- (c) 31
- (d) 18

Ans: C

61. When an atom loses an electron, the atom:

- (a) Becomes positively charged
- (b) Disintegrates
- (c) Experiences no effect at all
- (d) Becomes negatively charged

Ans: A

62. The energy used by a 1.5kW heater in 5 minutes is:

- (a) 5 J
- (b) 450 J
- (c) 7500 J
- (d) 450 000 J

Ans: D

63. The unit of resistivity is:

- (a) ohms
- (b) ohm millimetre
- (c) ohm metre
- (d) ohm/metre

Àns: C

64.A resistor marked as4K7G indicates a value of:

(a) 47Ω ±20%

(b) 4.7Ω k ±20% (c) 0.47Ω ±10%

(d) 4.7 kΩ ±2

Ans: D

65. The resistance of a 2 km length of cable of cross-sectional area $2mm^2$ and resistivity of $2 \times 10^{-8} \Omega$ m is:

- (a) 0.02Ω
- (b) 20Ω
- (c) 0.02mΩ
- (d) 200Ω

Ans: B

66. A piece of graphite has a cross-sectional area of $10mm^2$. If its resistance is 0.1Ω and its resistivity $10 \times 10^8 \Omega m$, its length is:

(a) 10 km

(b) 10 cm

(c) 10 mm

(d) 10 m

Ans: D

67. A nickel coil has a resistance of 13Ω at 50° C. If the temperature coefficient of resistance at 0° C is 0.006/ °C, the resistance at 0° C is:

- (a) 16.9Ω
- (b) 10Ω
- (c) 43.3Ω
- (d) 0.1Ω

Ans: B

68. A coil of wire has a resistance of 10 at 0°C. If the temperature coefficient of resistance for the wire is 0.004/ °C, its resistance at 100°C is:

- (a) 0.4Ω
- (b) 1.4Ω
- (c) 14Ω
- (d) 10Ω

Ans: C

69A colour coding of red-violet-black on a resistor indicates a value of:

- (a) 27Ω ±20%
- (b) 270Ω
- (c) 270Ω ±20%
- (d) 27Ω ±10%

Ans: C

70. An inductance of 10mH connected across a 100V, 50 Hz supply has an inductive reactance of

- (a) 10π
- (b) 1000π
- (c) π
- (d) π H
- Ans:C